




# Electric Current & DC Circuits



©2009 by Goodman & Zavorotniy

[www.njctl.org](http://www.njctl.org)

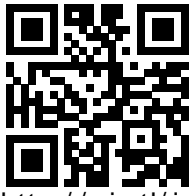

<http://njctl.org>



## **New Jersey Center for Teaching and Learning**

### **Progressive Science Initiative**

This material is made freely available at [www.njctl.org](http://www.njctl.org) and is intended for the non-commercial use of students and teachers. These materials may not be used for any commercial purpose without the written permission of the owners. NJCTL maintains its website for the convenience of teachers who wish to make their work available to other teachers, participate in a virtual professional learning community, and/or provide access to course materials to parents, students and others.

**Click to go to website:**  
**[www.njctl.org](http://www.njctl.org)**

## How to Use this File

- Each topic is composed of brief direct instruction
- There are formative assessment questions after every topic denoted by black text and a number in the upper left.
  - > Students work in groups to solve these problems but use student responders to enter their own answers.
  - > Designed for SMART Response PE student response systems.
  - > Use only as many questions as necessary for a sufficient number of students to learn a topic.
- Full information on how to teach with NJCTL courses can be found at [njctl.org/courses/teaching methods](http://njctl.org/courses/teaching methods)

# Electric Current & DC Circuits

*Click on the topic to go to that section*

- **Circuits**
- **Conductors**
- **Resistivity and Resistance**
- **Circuit Diagrams**
- **Measurement**



<http://njc.tl/n3>

# Circuits

**Return to  
Table of  
Contents**



<http://njc.tl/n3>


# Circuits

So do positive or negative charges flow through the circuit?

Historically, positive charges were identified as the ones that flowed in the circuit. It was not until a later time that we understood that it was the negative charge (electrons) which were free to move.

In reality, electrons flow from the negative terminal of the battery, through a conductor, to the positive terminal.

This is the actual current.

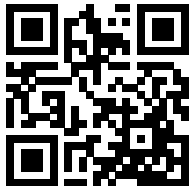


<http://njc.tl/n3>

# Current

While actual current is the flow of electrons from the negative terminal to the positive terminal, we use conventional current to model electric circuits.

Conventional current is the flow of positive charges flowing from the positive to the negative terminal.

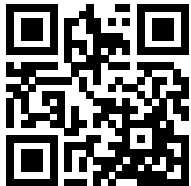Going forward, we will use conventional current to discuss electric circuits. Both conventional current and actual current lead to the same predictions but flow in opposite directions.





# Circuits

An electric circuit is an external path that charges can follow between two terminals using a conducting material.

For charge to flow, the path must be complete and unbroken.

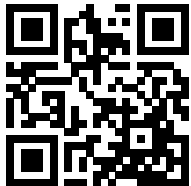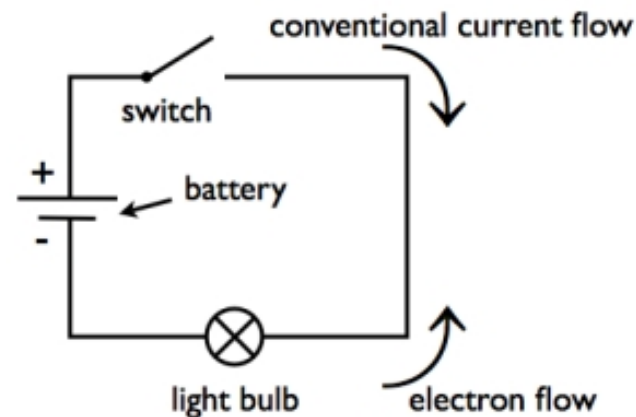An example of a conductor used to form a circuit is copper wire. You can think of a wire as a pipe for charge to move through.






# Current

The letter "I" is the symbol for current. It is defined as the amount of charge that flows past a location in a conductor per unit time.

$$I = \frac{\Delta Q}{\Delta t}$$

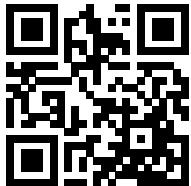$\Delta Q$  is the amount of charge, and  $\Delta t$  is the time it flowed past the location.




# Current

The current,  $I = \frac{\Delta Q}{\Delta t}$  has the units Coulombs per second.

The units can be rewritten as Amperes (A).


$$1 \text{ A} = 1 \text{ C/s}$$

Amperes are often called "amps".

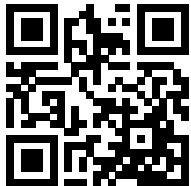

- 1 12 C of charge passes a location in a circuit in 10 seconds. What is the current flowing past the point?


**Answer**

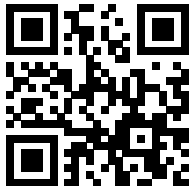

<http://njc.tl/n4>

2 20 C of charge passes a location in a circuit in 30 seconds. What is the current flowing past the point?


**Answer**

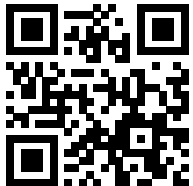

<http://njc.tl/n5>

3 A circuit has 3 A of current. How long does it take 45 C of charge to travel through the circuit?


**Answer**

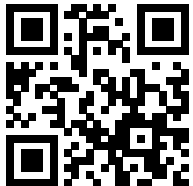

<http://njc.tl/n6>

4 A circuit has 10 A of current. How long does it take 20 C of charge to travel through the circuit?


**Answer**

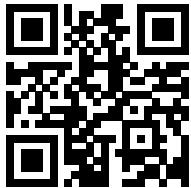

<http://njc.tl/n7>

5 A circuit has 10 A of current. How much charge travels through the circuit after 20s?

**Answer**

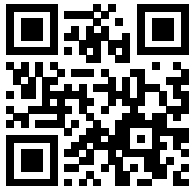

<http://njc.tl/n5>

6 A circuit has 2.5 A of current. How much charge travels through the circuit after 4s?

**Answer**



<http://njc.tl/n8>




# Batteries


Each battery has two terminals which are conductors. The terminals are used to connect an external circuit allowing the movement of charge.

Batteries convert chemical energy to electrical energy which maintains the potential difference.

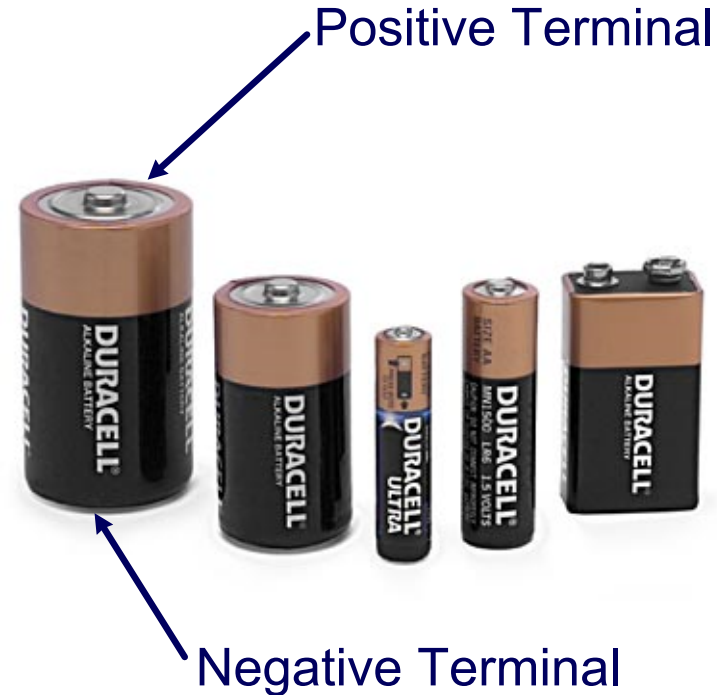The chemical reaction acts like an escalator, carrying charge up to a higher voltage.



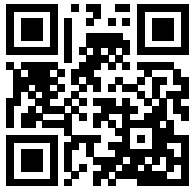[Click here for a Battery Voltage Simulation from PhET](http://njc.tl/n9)



<http://njc.tl/n9>

# Reviewing Basic Circuits

The circuit cannot have gaps.

The bulb had to be between the wire and the terminal.

A voltage difference is needed to make the bulb light.

The bulb still lights regardless of which side of the battery you place it on.


*As you watch the video, observations and the answers to the questions below.*

*What is going on in the circuit?*

*What is the role of the battery?*

*How are the circuits similar? different?*

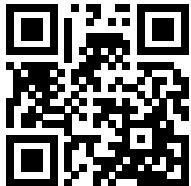Click here for  
video using the  
circuit simulator  
from PhET



<http://njc.tl/n9>


# Batteries and Current

The battery pushes current through the circuit. A battery acts like a pump, pushing charge through the circuit. It is the circuit's energy source.

Charges do not experience an electrical force unless there is a difference in electrical potential (voltage). Therefore, batteries have a potential difference between their terminals. The positive terminal is at a higher voltage than the negative terminal.

[click here for a video from Veritasium's Derek on current](#)


*How will voltage affect current?*

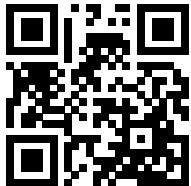

<http://njc.tl/n9>

# Conductors

**Return to  
Table of  
Contents**

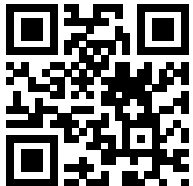

<http://njc.tl/na>


# Conductors

Some conductors "conduct" better or worse than others. Reminder: conducting means a material allows for the free flow of electrons.

The flow of electrons is just another name for current. Another way to look at it is that some conductors resist current to a greater or lesser extent.

We call this resistance,  $R$ . Resistance is measured in ohms which is noted by the Greek symbol omega ( $\Omega$ )

*How will resistance affect current?*

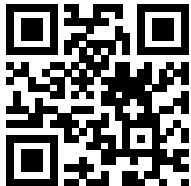

<http://njc.tl/na>

Click here to run another  
PhET simulation

# Current vs Resistance & Voltage

Raising resistance reduces current.

Raising voltage increases current.


We can combine these relationships in what we call  
"Ohm's Law".

$$I = \frac{V}{R}$$

Another way to write this is that:

$$R = \frac{V}{I} \quad \text{OR} \quad V = IR$$

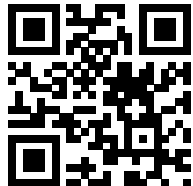You can see that one  $\Omega = \frac{V}{A}$




<http://njc.tl/na>

[click here for a Veritasium  
music video on electricity](#)

- 7 A flashlight has a resistance of  $25\ \Omega$  and is connected by a wire to a  $120\ \text{V}$  source of voltage. What is the current in the flashlight?


**Answer**

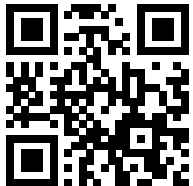

<http://njc.tl/nb>

- 8 A flashlight has a resistance of  $30\ \Omega$  and is connected by a wire to a  $90\ \text{V}$  source of voltage. What is the current in the flashlight?

**Answer**

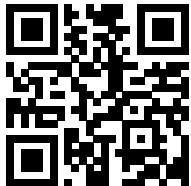



9 What is the current in a wire whose resistance is  $3\ \Omega$  if  $1.5\ \text{V}$  is applied to it?


**Answer**



<http://njc.tl/nd>

10 How much voltage is needed in order to produce a 0.70 A current through a 490  $\Omega$  resistor?


**Answer**

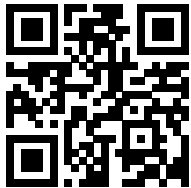

<http://njc.tl/ne>

11 How much voltage is needed in order to produce a 0.5 A current through a 150  $\Omega$  resistor?


**Answer**

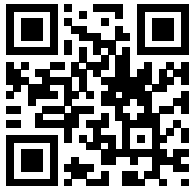

<http://njc.tl/nf>

12 What is the resistance of rheostat coil, if 0.05 A of current flows through it when 6 V is applied across it?


**Answer**

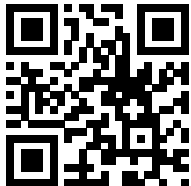

<http://njc.tl/ng>

13 What is the resistance of arheostat coil, if 20 A of current flows through it when 1000 V is applied across it?

**Answer**

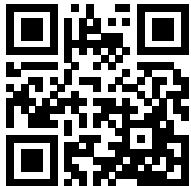

<http://njc.tl/nh>

# Electrical Power

Power is defined as work per unit time

$$P = \frac{W}{t}$$

if  $W = QV$  then substitute:


$$P = \frac{QV}{t}$$

if  $I = \frac{Q}{t}$  then substitute:

$$P = IV$$

*What happens if the current is increased?*

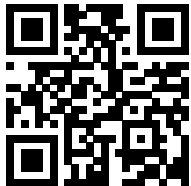*What happens if the voltage is decreased?*





<http://njc.tl/ni>

# Electrical Power

Let's think about this another way...

The water at the top has GPE & KE.

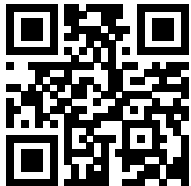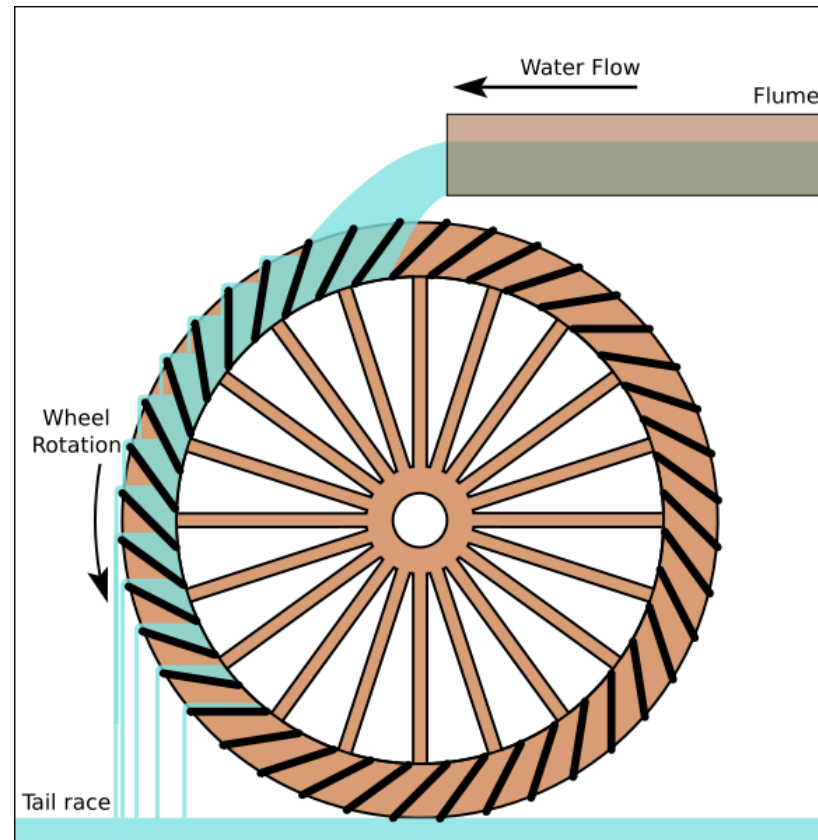As the water falls, it loses GPE and the wheel gets turned, doing work. When the water falls to the bottom it is now slower, having done work.




<http://njc.tl/ni>

# Electrical Power


Electric circuits are similar.

A charge falls from high voltage to low voltage.

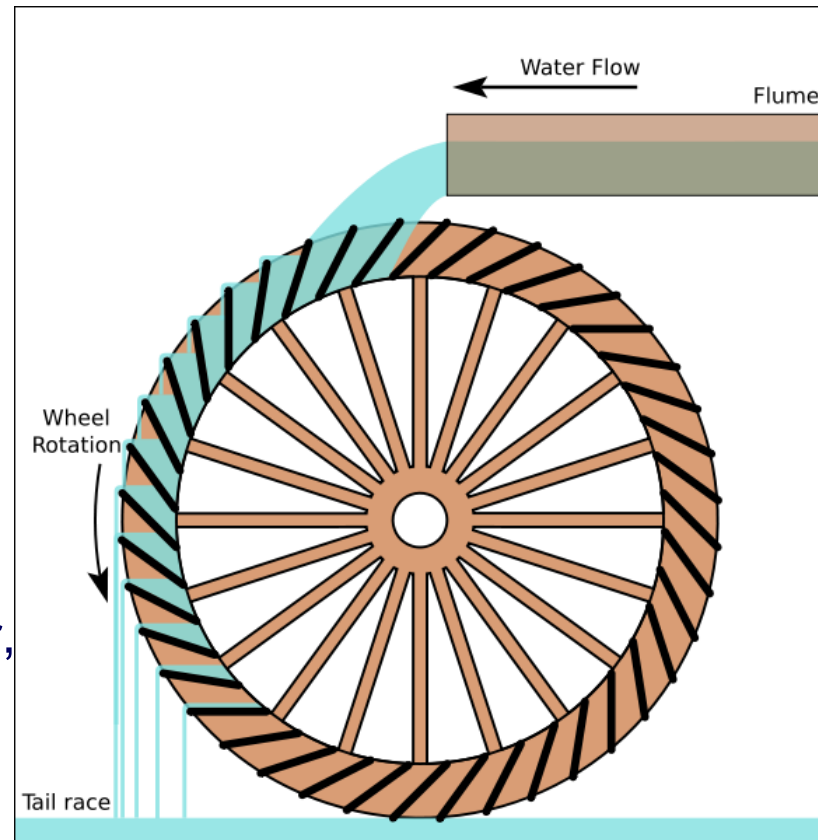In the process of falling energy may be used (light bulb, run a motor, etc).



*What is the unit of Power?*

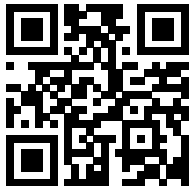

<http://njc.tl/ni>



# Electrical Power

How can we re-write electrical power by using Ohm's Law?

(electrical power)


$$P = IV$$

(Ohm's Law)

$$I = \frac{V}{R}$$

$$P = \frac{VV}{R}$$

$$P = \frac{V^2}{R}$$

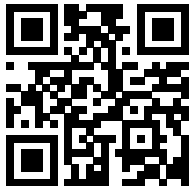

# Electrical Power

Is there yet another way to rewrite this?

$$I = \frac{V}{R} \text{ can be rewritten as } V = IR.$$

(electrical power)

$$P = IV$$

(Ohm's Law)

$$V = IR$$

*We can substitute this into Power*

$$P = I(IR)$$

$$P = I^2 R$$




<http://njc.tl/ni>

# Batteries

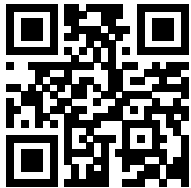**D****C****AAA****AA****1.5 V****9 V**

D, C, AA, & AAA have the same voltage, however they differ in the amount of power they deliver.


For instance, D batteries can deliver more current and therefore more power.



<http://njc.tl/ni>

- 14 A toy car's electric motor has a resistance of  $17\ \Omega$ ; find the power delivered to it by a 6-V battery.


**Answer**

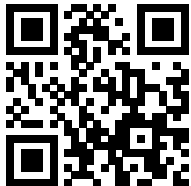

<http://njc.tl/nj>

- 15 A toy car's electric motor has a resistance of  $6\ \Omega$ ; find the power delivered to it by a 7-V battery.


**Answer**

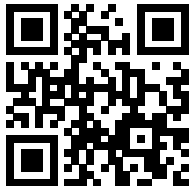

<http://njc.tl/nk>

16 What is the power consumption of a flash light bulb that draws a current of 0.28 A when connected to a 6 V battery?


**Answer**

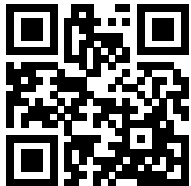

<http://njc.tl/nl>

17 What is the power consumption of a flash light bulb that draws a current of 0.33 A when connected to a 100 V battery?


**Answer**

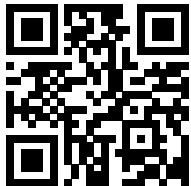

<http://njc.tl/nm>

18 A  $30\Omega$  toaster consumes 560 W of power: how much current is flowing through the toaster?

**Answer**

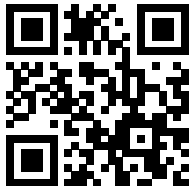


<http://njc.tl/nn>



19 A  $50\Omega$  toaster consumes 200 W of power: how much current is flowing through the toaster?

**Answer**

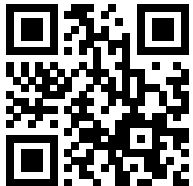

<http://njc.tl/no>

20 When 30 V is applied across a resistor it generates 600 W of heat: what is the magnitude of its resistance?


**Answer**



<http://njc.tl/np>

21 When 100 V is applied across a resistor it generates 200 W of heat: what is the magnitude of its resistance?

**Answer**

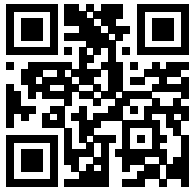

<http://njc.tl/nq>

## "Pipe" size


How could the wire in the circuit affect the current?

If wire is like a pipe, and current is like water that flows through the pipe...

if there were pipes with water in them, what could we do to the pipes to change the speed of the water (the current)?



**Answer**

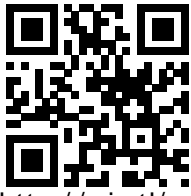

<http://njc.tl/nr>

# Resistivity and Resistance



<http://njc.tl/nr>

**Return to  
Table of  
Contents**

# Resistivity & Resistance


Every conductor "conducts" electric charge to a greater or lesser extent.

The last example also applies to conductors like copper wire. Decreasing the length (L) or increasing the cross-sectional area (A) would increase conductivity.

Also, the measure of a conductor's resistance to conduct is called its resistivity. Each material has a different resistivity.

Resistivity is abbreviated using the Greek letter rho ( $\rho$ ).

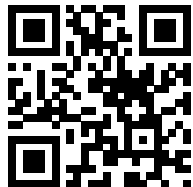Combining what we know about A, L, and  $\rho$ , we can find a conductor's total resistance.



<http://njc.tl/nr>

$$R = \frac{\rho L}{A}$$

# Resistivity & Resistance

$$R = \frac{\rho L}{A}$$

Resistance,  $R$ , is measured in Ohms ( $\Omega$ ).  $\Omega$  is the Greek letter Omega.

Cross-sectional area,  $A$ , is measured in  $\text{m}^2$

Length,  $L$ , is measured in  $\text{m}$

Resistivity,  $\rho$ , is measured in  $\Omega\text{m}$

*How can we define  $A$  for a wire?*



<http://njc.tl/nr>


# Resistance

$$\rho = \frac{RA}{L}$$

What is the resistance of a good conductor?

Low; low resistance means that electric charges are free to move in a conductor.

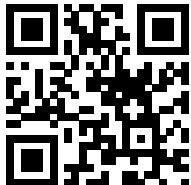[Click here for a PhET simulation about Resistance](#)



<http://njc.tl/nr>



## Resistivities of Common Conductors


Material	Resistivity ( $10^{-8} \Omega\text{m}$ )
Silver	1.59
Copper	1.68
Gold	2.44
Aluminum	2.65
Tungsten	5.60
Iron	9.71
Platinum	10.6
Mercury	98
Nichrome	100

22 Rank the following materials in order of best conductor to worst conductor.

- ☐ A Iron, Copper, Platinum
- ☐ B Platinum, Iron, Copper
- ☐ C Copper, Iron, Platinum

Material	Resistivity ( $10^{-8} \Omega\text{m}$ )
Silver	1.59
Copper	1.68
Gold	2.44
Aluminum	2.65
Tungsten	5.60
Iron	9.71
Platinum	10.6
Mercury	98
Nichrome	100


Answer

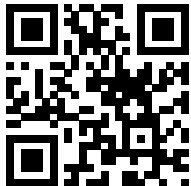

<http://njc.tl/nr>

23 What is the resistance of a 2 m long copper wire whose cross-sectional area of  $0.2 \text{ mm}^2$ ?


**Answer**

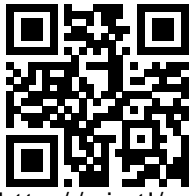

<http://njc.tl/ns>

24 An aluminum wire with a length of 900 m and cross-sectional area of  $10 \text{ mm}^2$  has a resistance of  $2.5 \Omega$ . What is the resistivity of the wire?

**Answer**

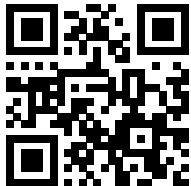

<http://njc.tl/nt>

25 What diameter of 100 m long copper wire would have a resistance of  $0.10\ \Omega$ ?


**Answer**



<http://njc.tl/nu>

26 What is the cross-sectional area of a  $10\Omega$  copper wire of length is 10000 meters?

**Answer**

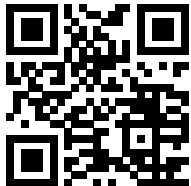

<http://njc.tl/nv>

27 What is the length of a  $10\ \Omega$  copper wire whose diameter is 3.2 mm?

**Answer**



# Circuit Diagrams

**Return to  
Table of  
Contents**



for more information




# Circuit Diagrams

Drawing realistic pictures of circuits can be very difficult.  
For this reason, we have common symbols to represent each piece.




**Resistor**

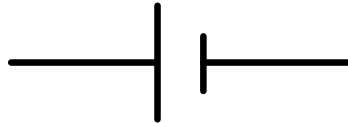

**Battery**



**Wire**

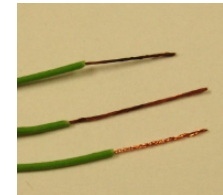


*\*Note: Circuit diagrams do not show where each part is physically located.*
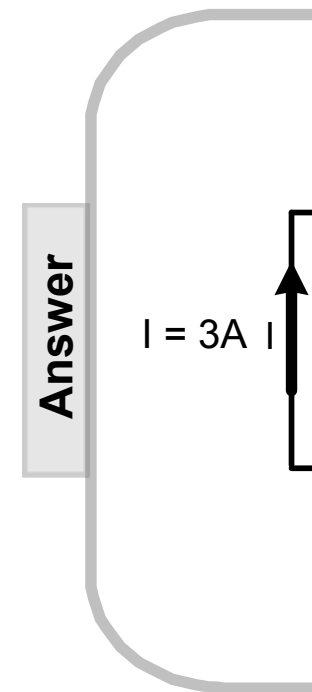
## Circuit Diagrams

Draw a simple circuit that has a 9 V battery with a 3  $\Omega$  resistor across its terminals. What is the magnitude and direction of the current?




*Conventional current flows from the positive terminal to the negative terminal.*



# Circuit Diagrams


There are two ways to add a second resistor to the circuit.

## Series

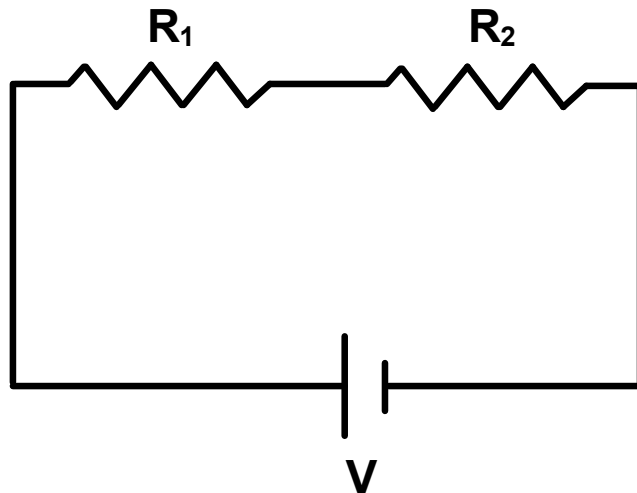

All charges must move through both resistors to get to the negative terminal.

## Parallel


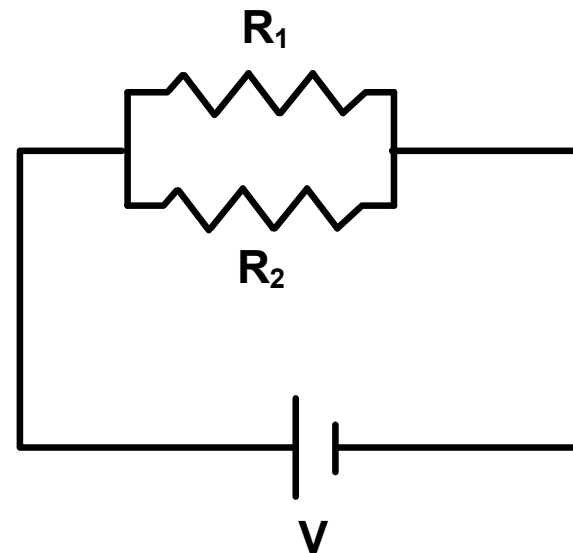


Charges pass through either  $R_1$  or  $R_2$  but not both.


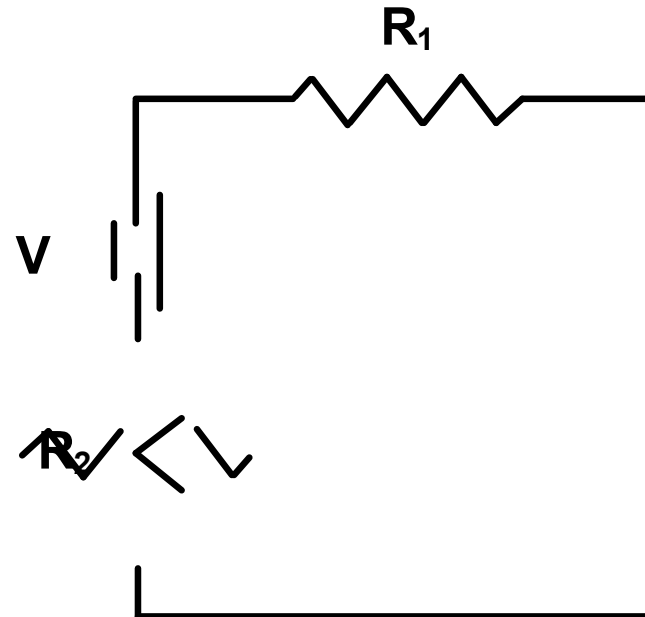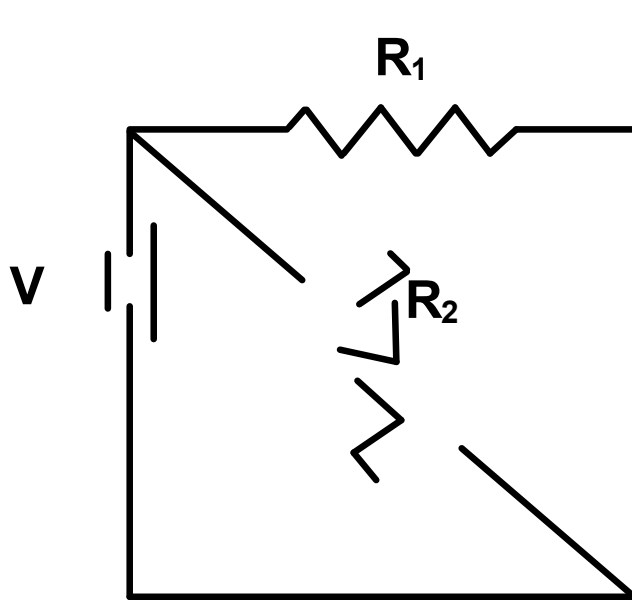
# Circuit Diagrams

Are the following sets of resistors in series or parallel?



**Answer**




# Equivalent Resistance

Resistors and voltage from batteries determine the current.


Circuits can be redrawn as if there were only a single resistor and battery. By reducing the circuit this way, the circuit becomes easier to study.

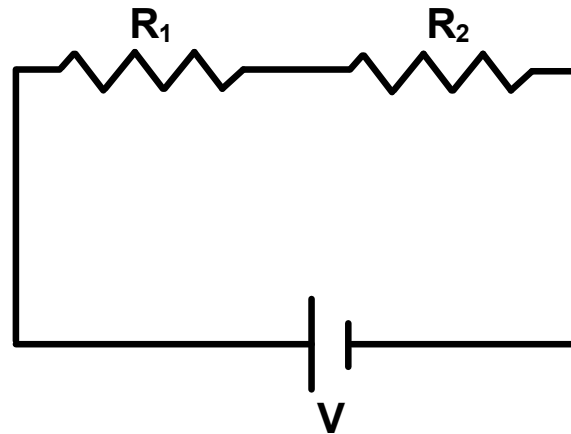The process of reducing the resistors in a circuit is called finding the equivalent resistance ( $R_{eq}$ ).


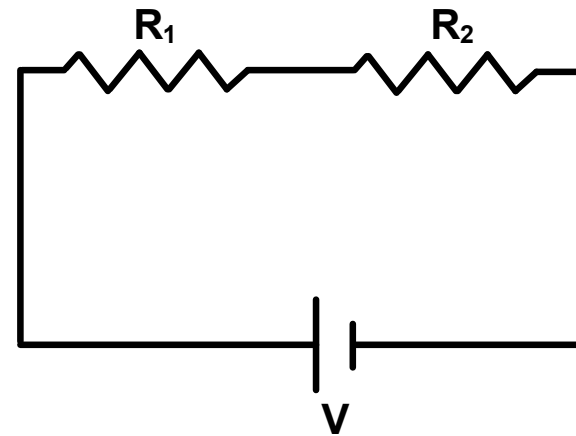
# Series Circuits: Equivalent Resistance

What happens to the current in the circuit to the right?




**Answer**


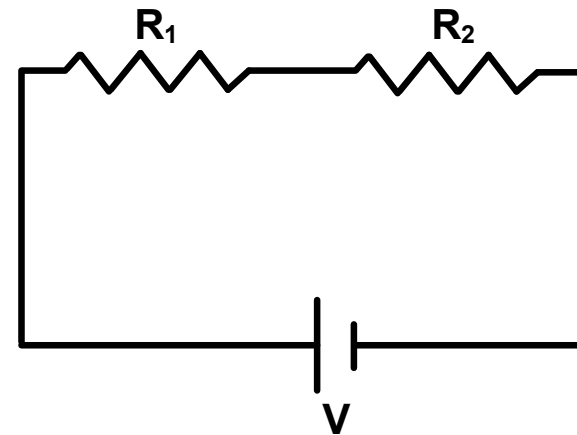
# Series Circuits: Equivalent Resistance

What happens to the voltage as it moves around the circuit?



**Answer**



# Series Circuits: Equivalent Resistance

If  $V = V_1 + V_2 + V_3 + \dots$

*substitute Ohm's Law solved for  $V$  is:  $V = IR$*

$IR = I_1R_1 + I_2R_2 + I_3R_3$

*but since current ( $I$ ) is the same everywhere in a series circuit,*

$IR = IR_1 + IR_2 + IR_3$

$I = I_1 = I_2 = I_3$

$R_{eq} = R_1 + R_2 + R_3 + \dots$


*Now divide by  $I$*



to find the equivalent resistance ( $R_{eq}$ ) of a series circuit, add the resistance of all the resistors. If you add more resistors to a series circuit, what happens to the resistance?



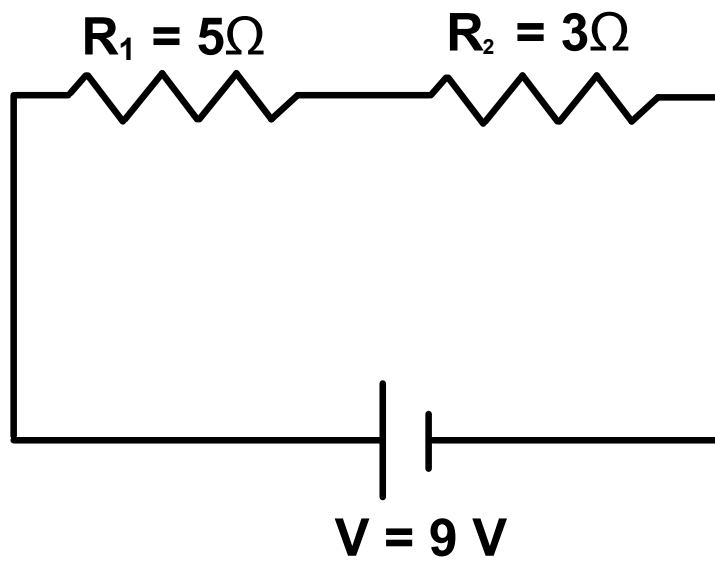
28 What is the equivalent resistance in this circuit?




Answer



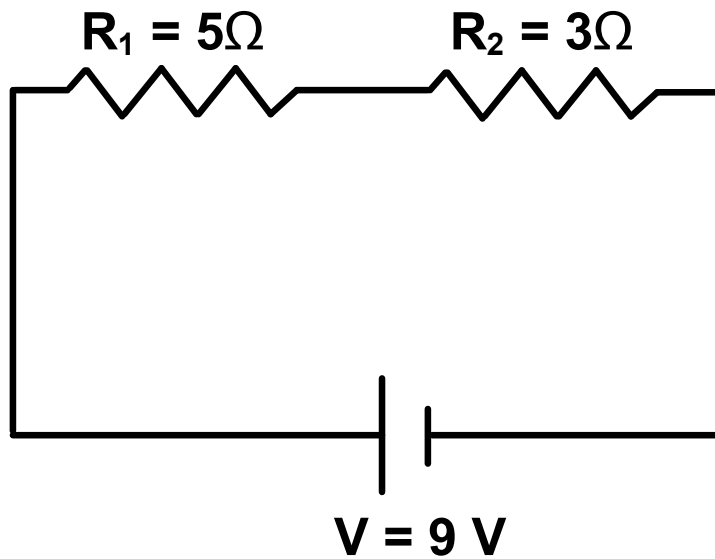29 What is the total current at any spot in the circuit?




**Answer**

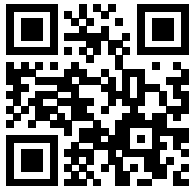

<http://njc.tl/nx>

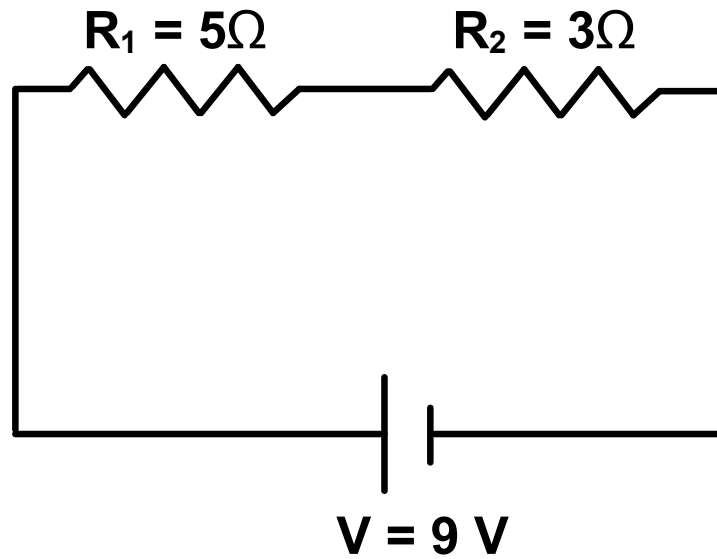30 What is the voltage drop across  $R_1$ ?




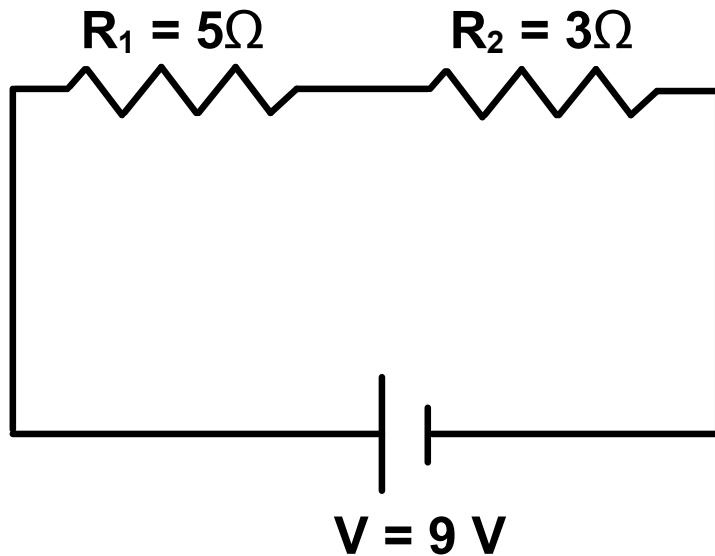**Answer**




<http://njc.tl/ny>

31 What is the voltage drop across  $R_2$ ?




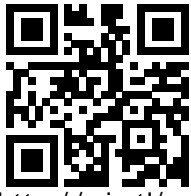**Answer**


*hint: A good way to check your work is to see if the voltage drop across all resistors equals the total voltage in the circuit.*



32 How much power is used by  $R_1$ ?

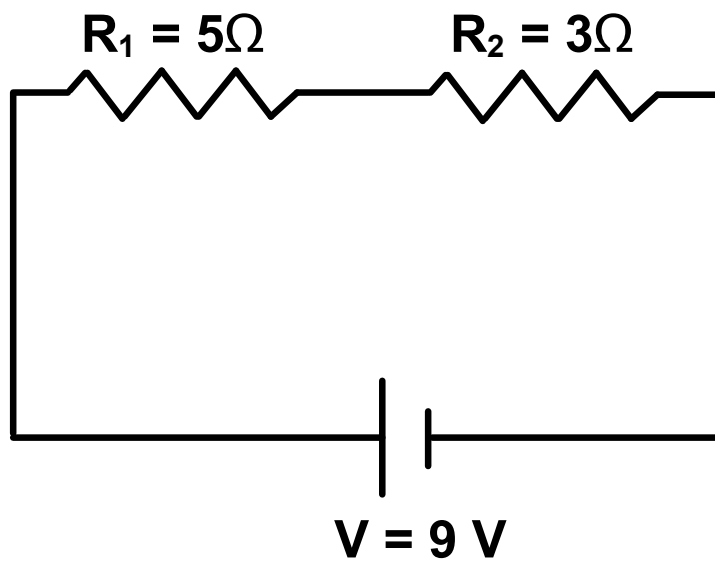


**Answer**

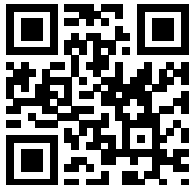


<http://njc.tl/o0>

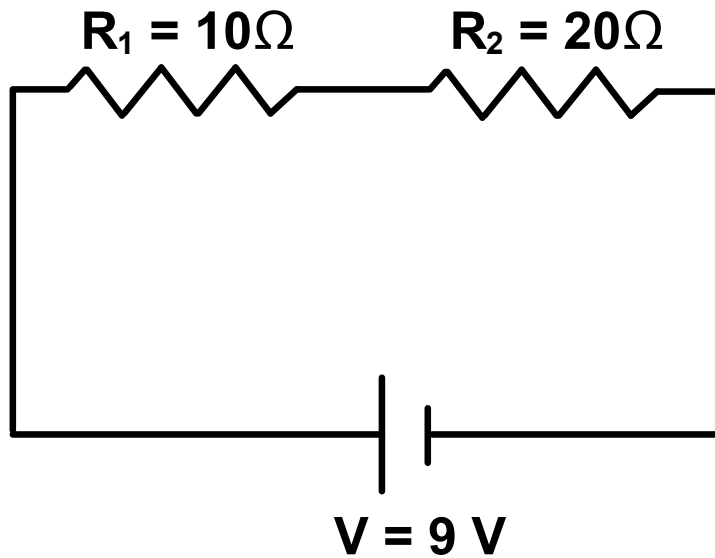33 What is the equivalent resistance in this circuit?




Answer

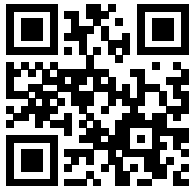


<http://njc.tl/o1>

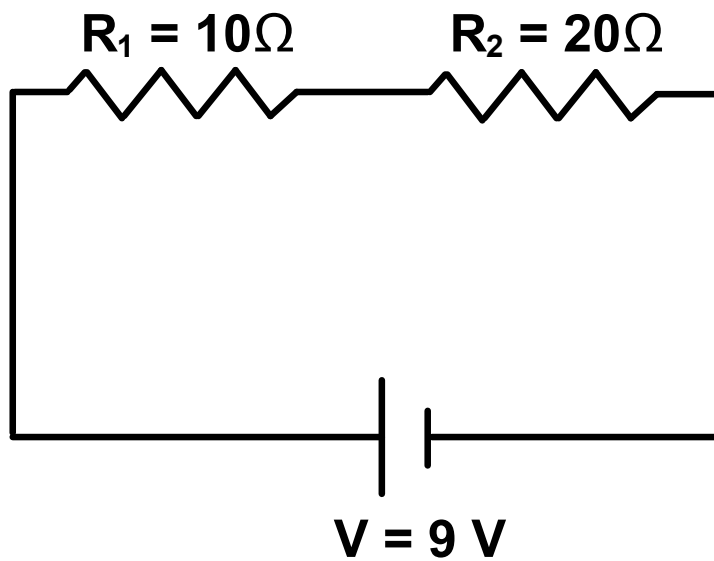34 What is the total current at any spot in the circuit?




Answer

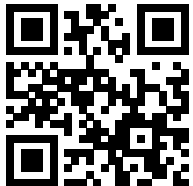


<http://njc.tl/o1>

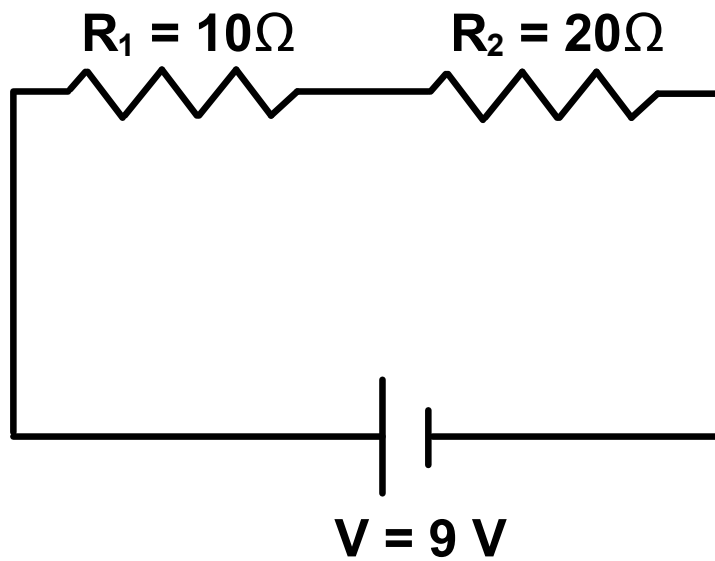35 What is the voltage drop across  $R_1$ ?




Answer

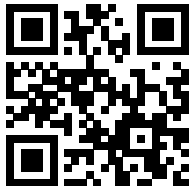


<http://njc.tl/o1>



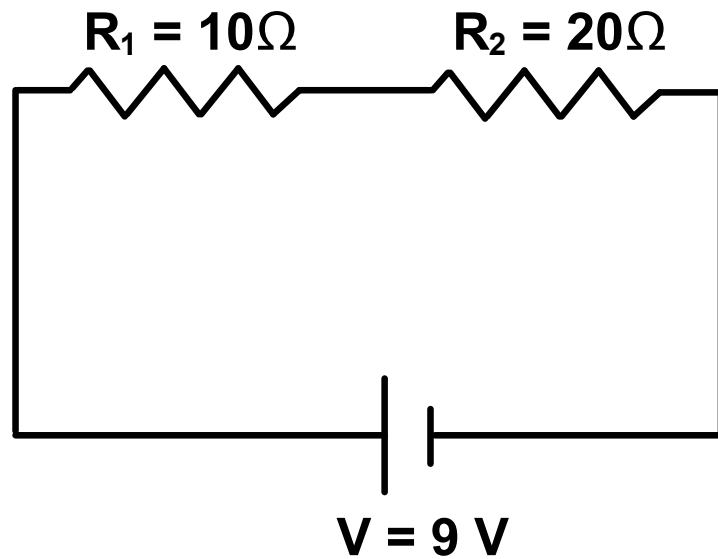
36 What is the voltage drop across  $R_2$ ?




Answer

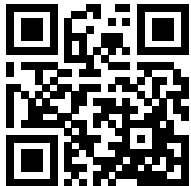

37 How much power is used by  $R_1$ ?

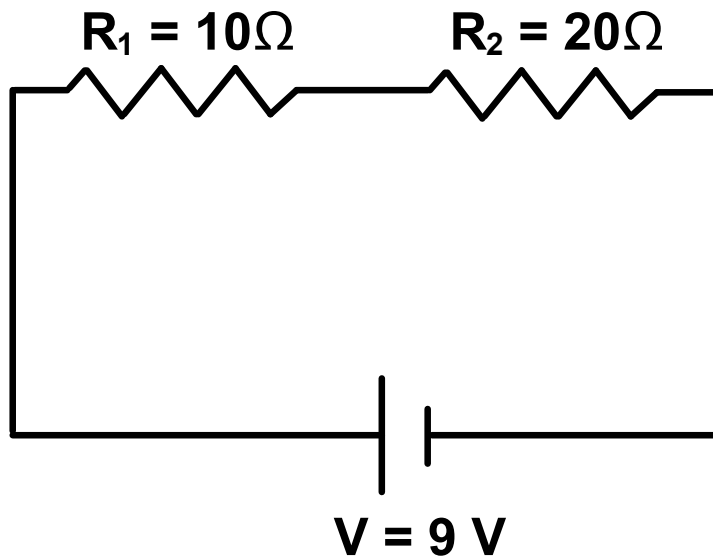


Answer

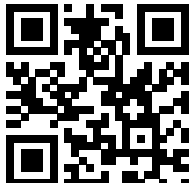


<http://njc.tl/o3>

38 How much power is used by  $R_2$ ?

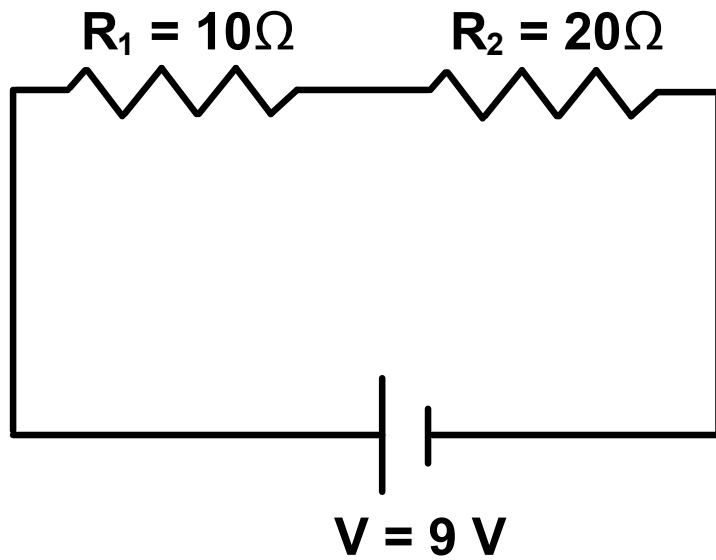


Answer

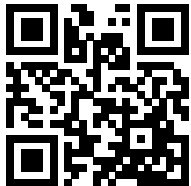


<http://njc.tl/o4>
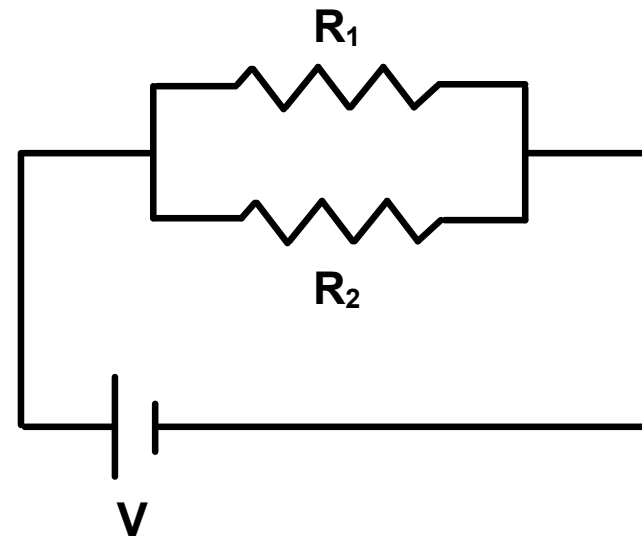
# Parallel Circuits: Equivalent Resistance

What happens to the current in the circuit to the right?




**Answer**

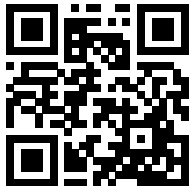

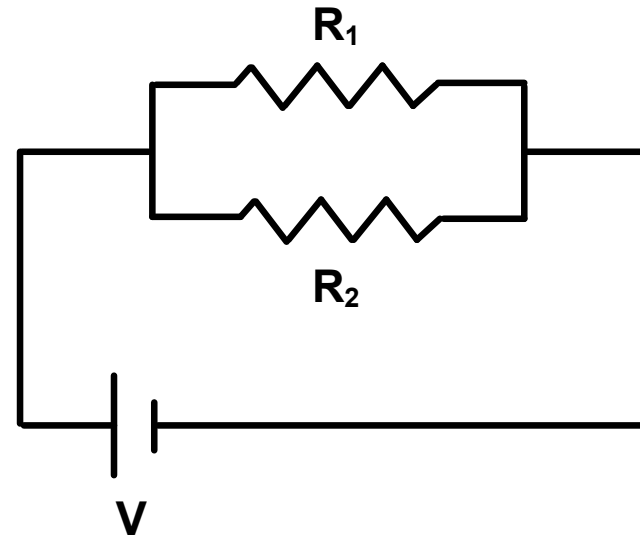
# Parallel Circuits: Equivalent Resistance

What happens to the voltage as it moves around the circuit?



Answer

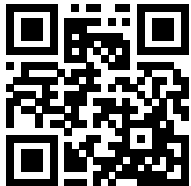

<http://njc.tl/o5>

# Parallel Circuits: Equivalent Resistance

$$\text{If } I = I_1 + I_2 + I_3$$

*Rewrite Ohm's Law for  $I$  and substitute for each resistor*

$$\frac{V}{R} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


*Also, since  $V = V_1 = V_2 = V_3$  so we can substitute  $V$  for any other voltage*

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

*Voltage is a common factor, so factor it out!*

$$\frac{V}{R} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

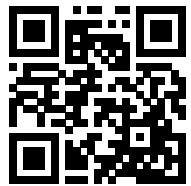*Divide by  $V$  to eliminate voltage from the equation.*




<http://njc.tl/o5>


$$+ \frac{1}{R_2} + \frac{1}{R_3}$$

*you add more resistors in parallel, what will happen ~~the~~ the resistance of the circuit?*

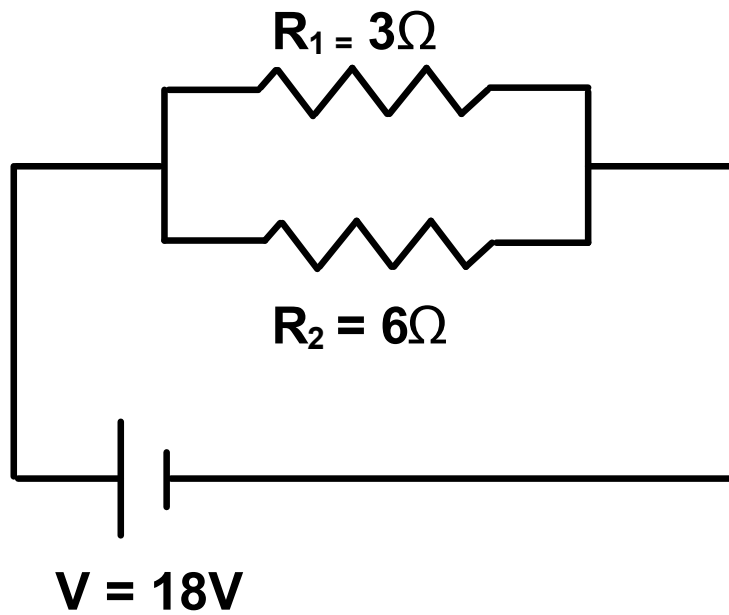
39 What is the equivalent resistance in the circuit?




**Answer**

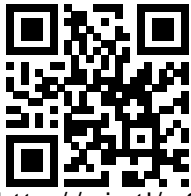

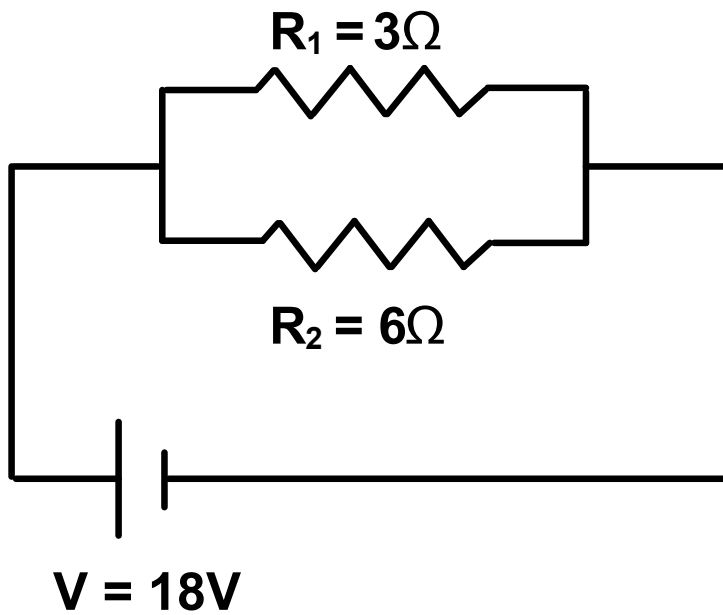40 What is the voltage at any spot in the circuit?




Answer

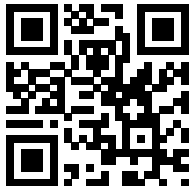


<http://njc.tl/o7>




41 What is the current through  $R_1$ ?

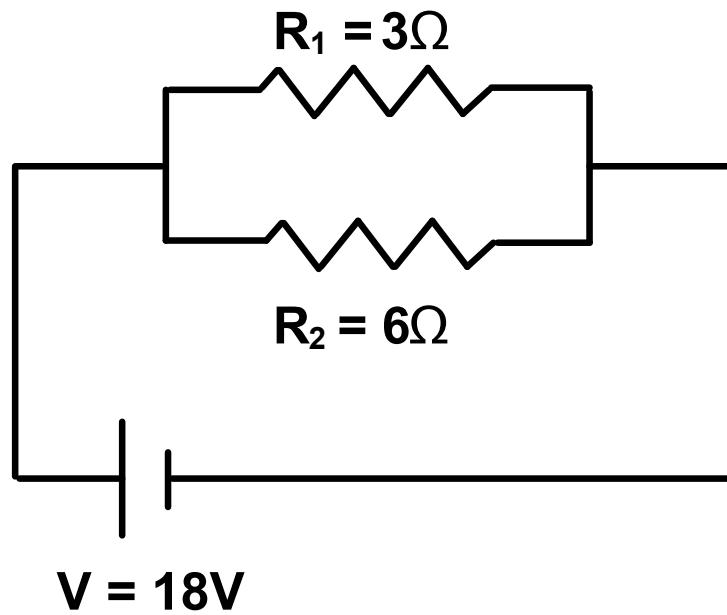


Answer

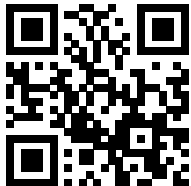


42 What is the current through  $R_2$ ?

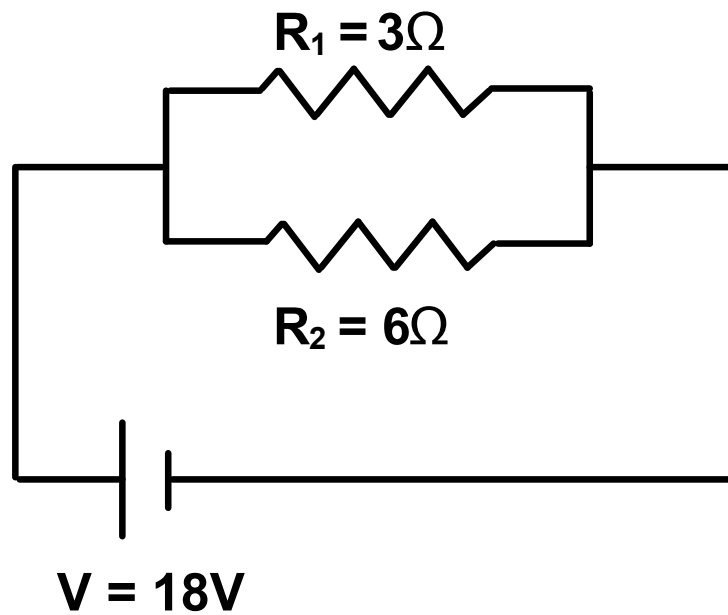


Answer

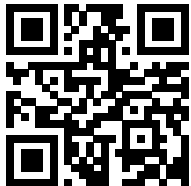


43 What is the power used by  $R_1$ ?

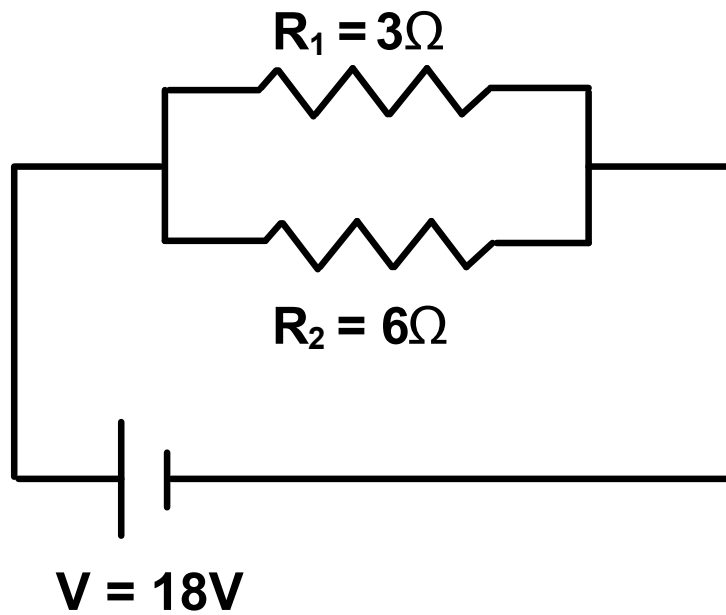


**Answer**

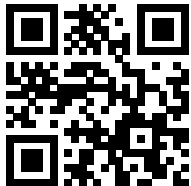


44 What is the power used by  $R_2$ ?

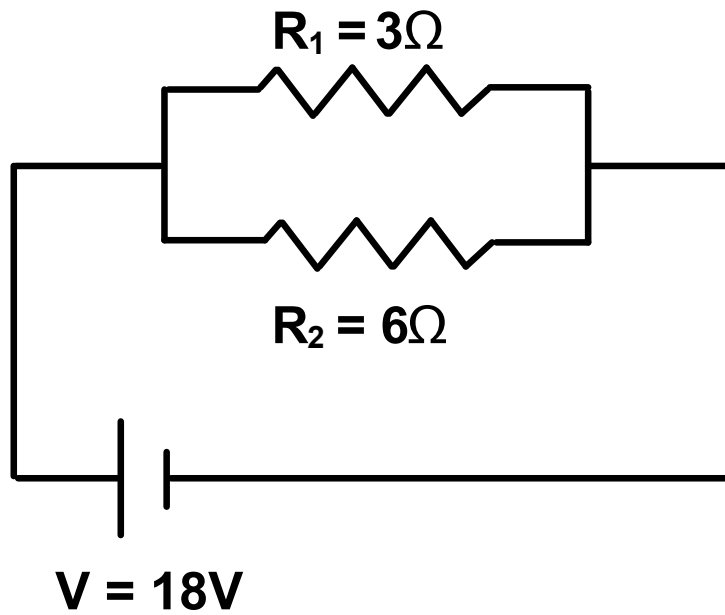

Answer

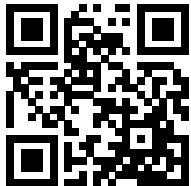

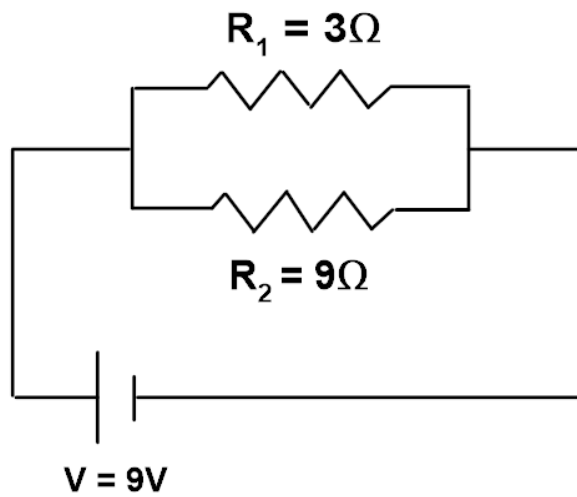
45 What is the equivalent resistance in the circuit?



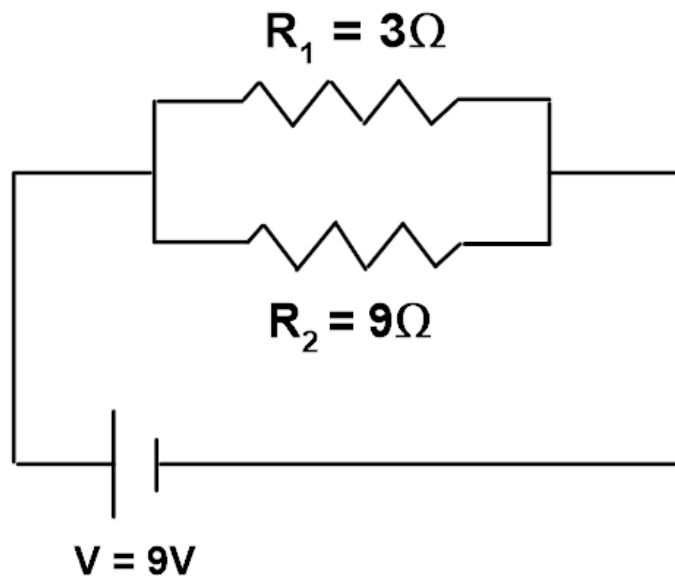
**Answer**



46 What is the voltage at any spot in the circuit?




Answer

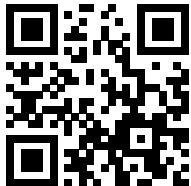


<http://njc.tl/od>

47 What is the current through  $R_1$ ?

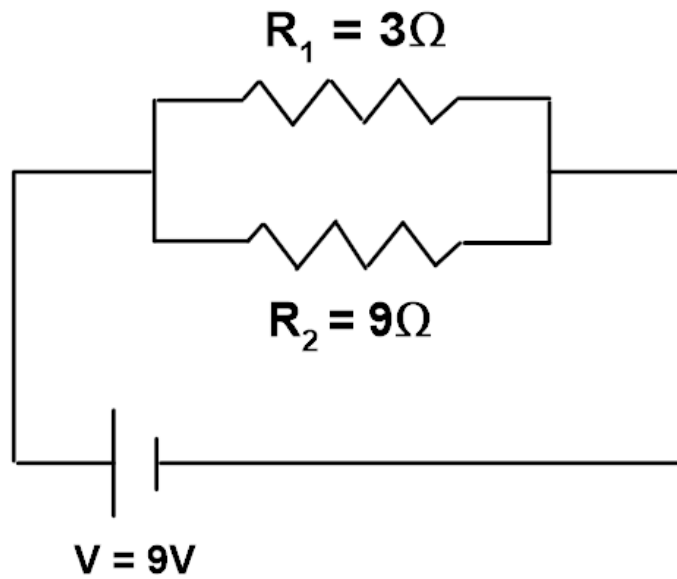


**Answer**

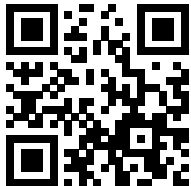

<http://njc.tl/od>

48 What is the current through  $R_2$ ?

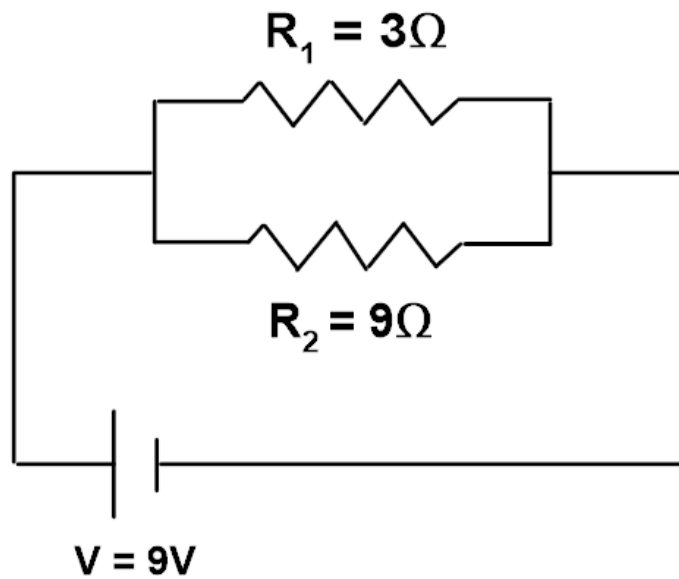


Answer






49 What is the power used by  $R_1$ ?

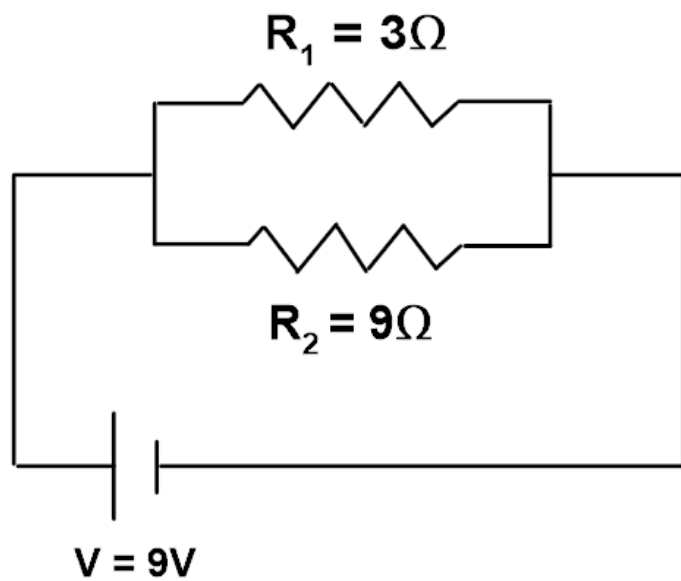


**Answer**

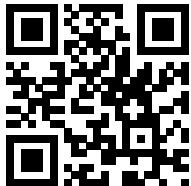

<http://njc.tl/of>

50 What is the power used by  $R_1$ ?

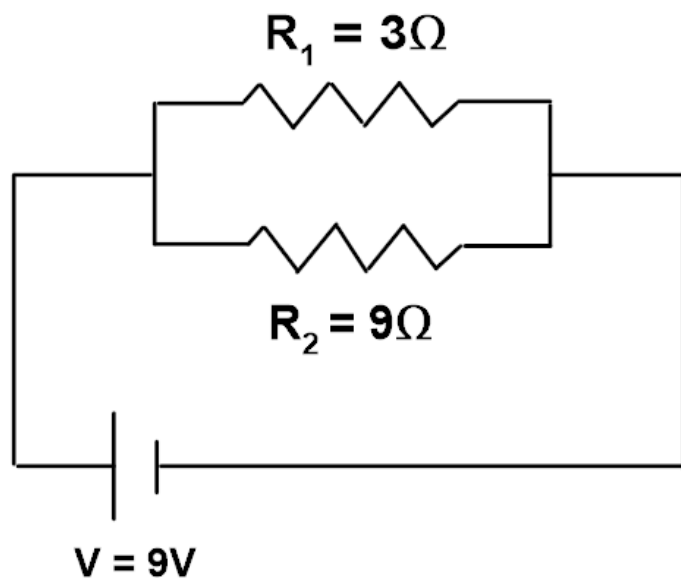


**Answer**



<http://njc.tl/og>


51 What is the power used by  $R_2$ ?

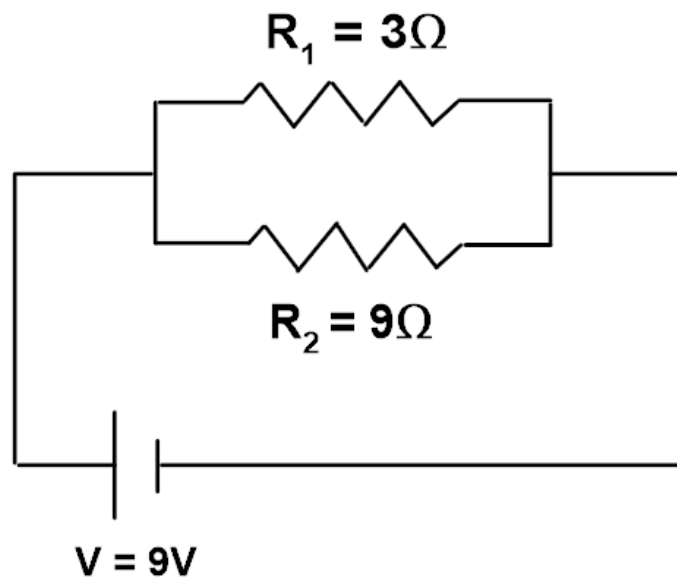

**Answer**


# Measurement

**Return to  
Table of  
Contents**

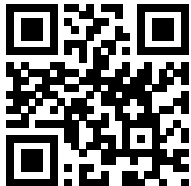

<http://njc.tl/oh>


# Voltmeter

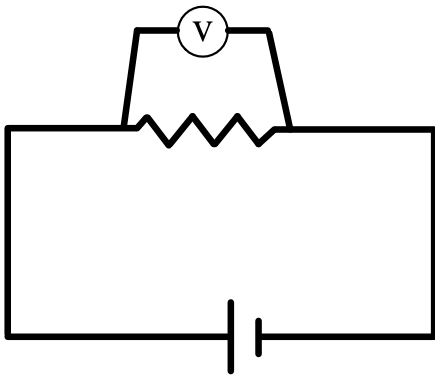


Voltage is measured with a voltmeter. Voltmeters are connected in parallel and measure the difference in potential between two points.

Since circuits in parallel have the same voltage, and a voltmeter has very high resistance, very little current passes through it.

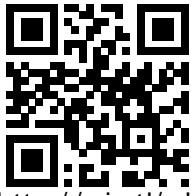This means that it has little effect on the circuit it.



<http://njc.tl/oh>


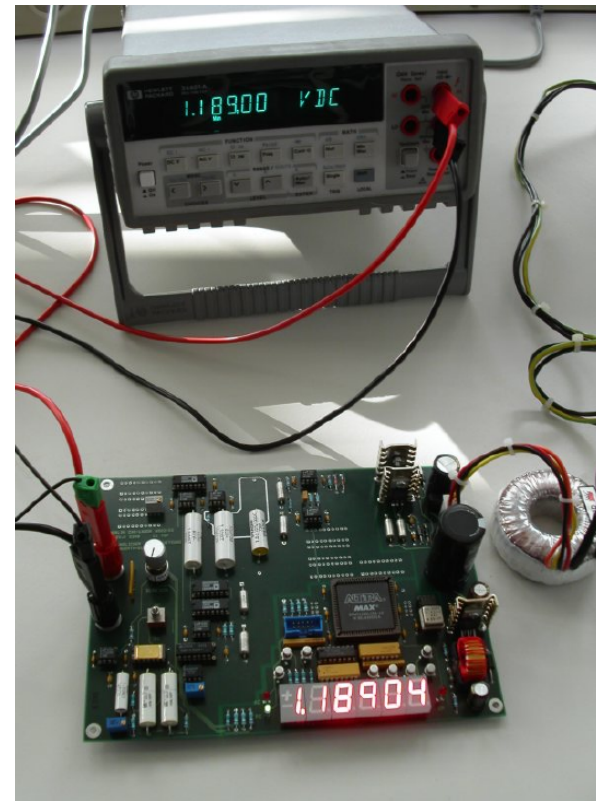

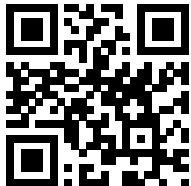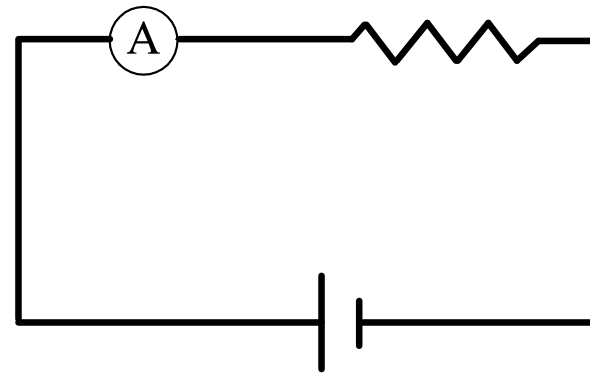
# Ammeter

Current is measured using an ammeter.



Ammeters are placed in series with a circuit. In order to not interfere with the current, the ammeter has a very low resistance.




<http://njc.tl/oh>

# Multimeter

Although there are separate items to measure current and voltage, there are devices that can measure both (one at a time).


These devices are called multimeters. Multimeters can also measure resistance.

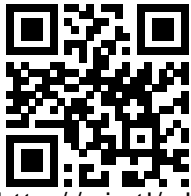[Click here for a PhET simulation on circuits](#)




<http://njc.tl/oh>

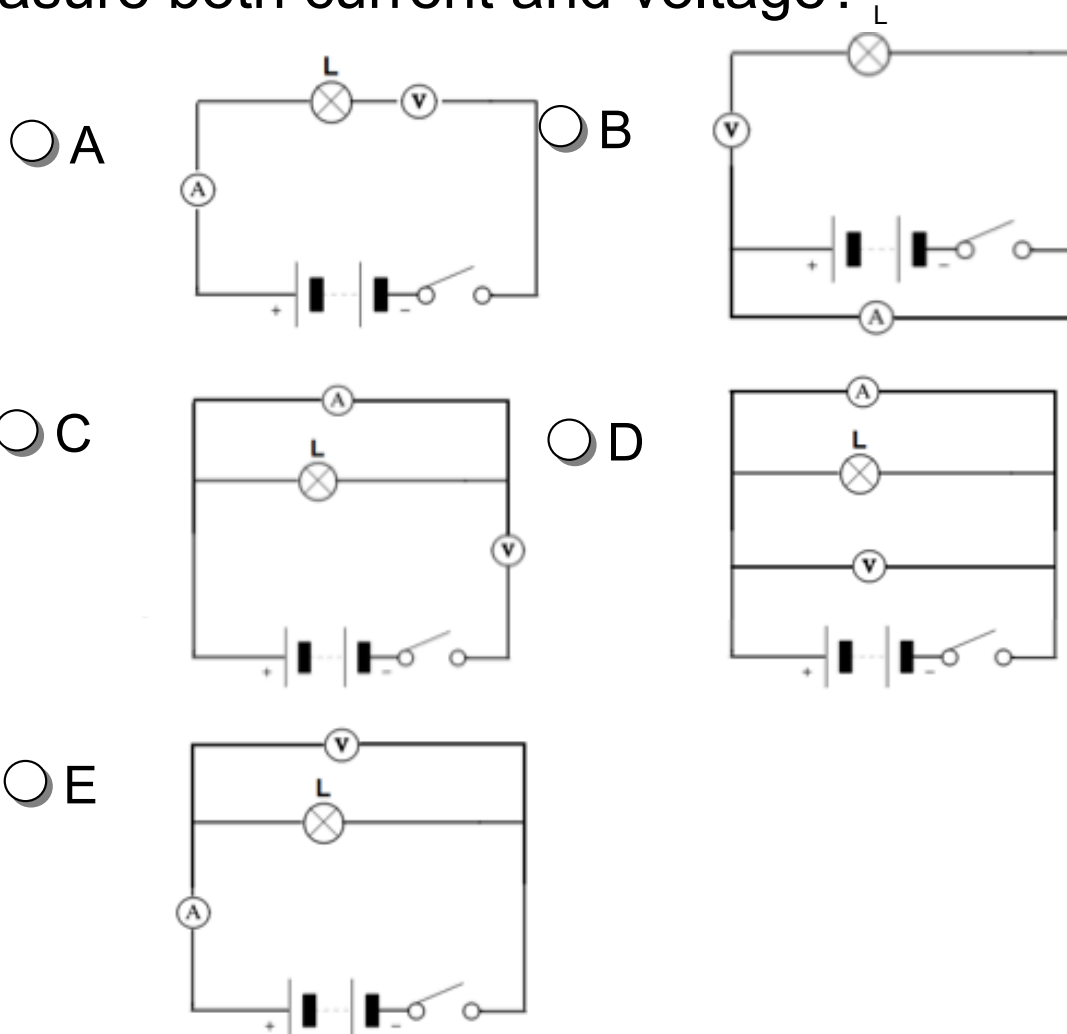52 A group of students prepare an experiment with electric circuits. Which of the following diagrams can be used to measure both current and voltage?




**Answer**

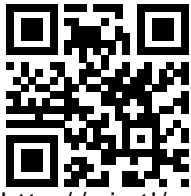

<http://njc.tl/oi>



# Electromotive Force

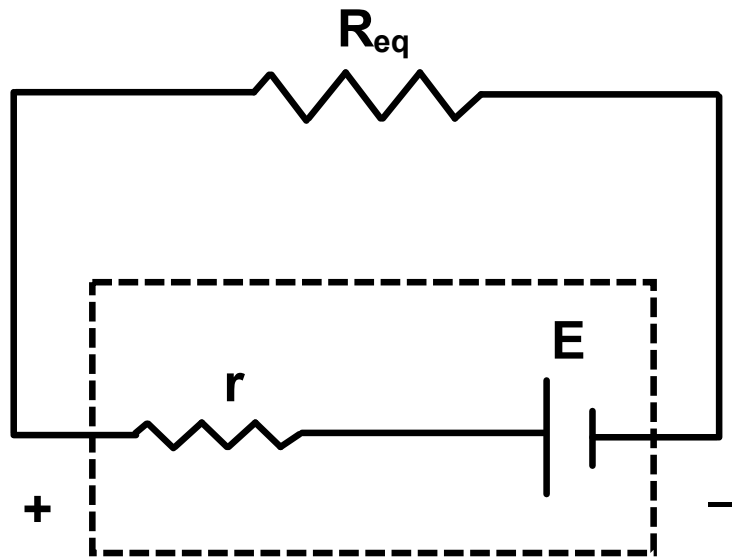

A battery is a source of voltage AND a resistor.

Each battery has a source of electromotive force and internal resistance.


Electromotive force (EMF) is the process that carries charge from low to high voltage.



<http://njc.tl/oj>

Another way to think about it is that EMF is the voltage you measure when no resistance is connected to the circuit.


# Electromotive Force

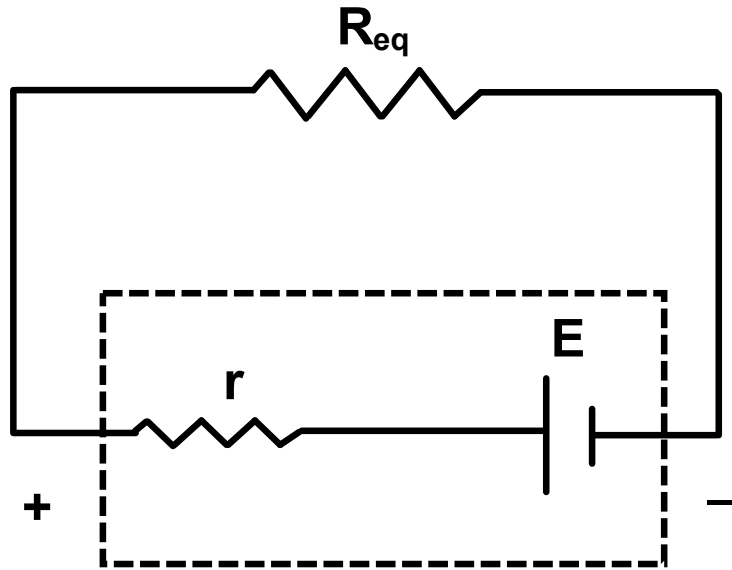


**Terminal voltage ( $V_T$ )** is the voltage measured when a voltmeter is across its terminals.

If there is no circuit attached, no current flows, and the measurement will equal the EMF.

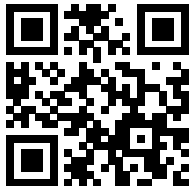If however a circuit is attached, the internal resistance will result in a voltage drop, and a smaller terminal voltage. ( $E - Ir$ )



# Terminal Voltage

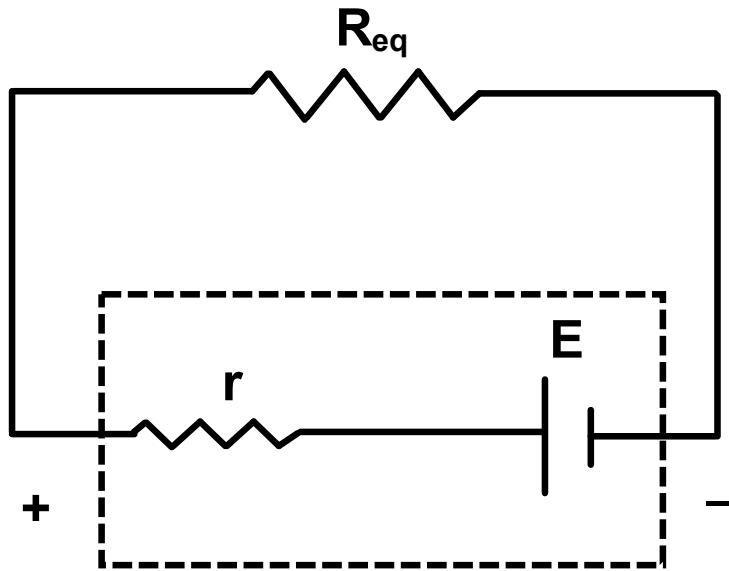


We say that the terminal voltage is:

$$V_T = E - Ir$$

Maximum current will occur when there is zero external current.

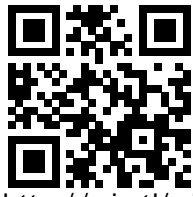When solving for equivalent resistance in a circuit, the internal resistance of the battery is considered a series resistor.




<http://njc.tl/oj>


$$R_{EQ} = R_{int} + R_{ext}$$

53 When the switch in the circuit below is open, the voltmeter reading is referred to as:

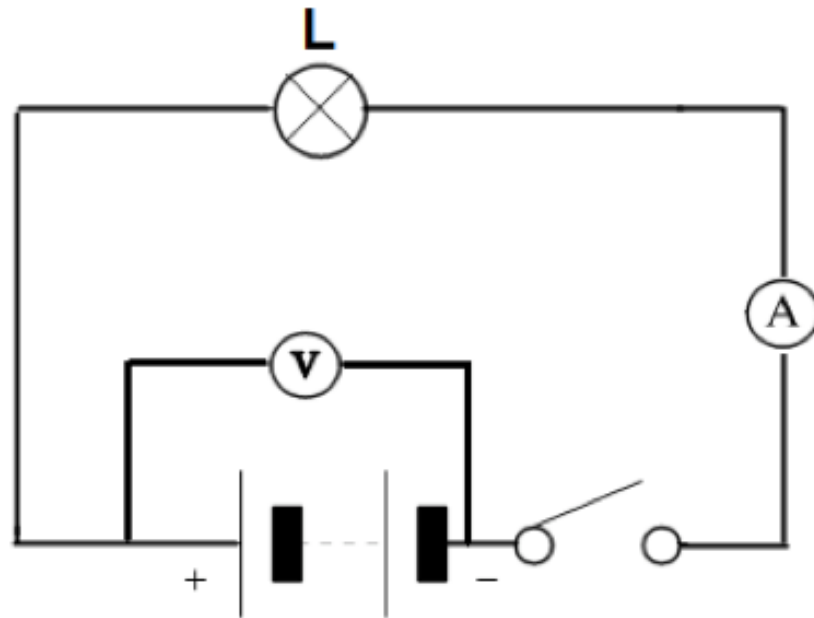- ☐ A EMF
- ☐ B Current
- ☐ C Power
- ☐ D Terminal Voltage
- ☐ E Restivity




Answer

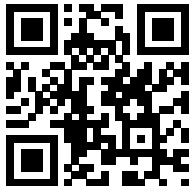


54 When the switch in the circuit below is closed, the voltmeter reading is referred to as:

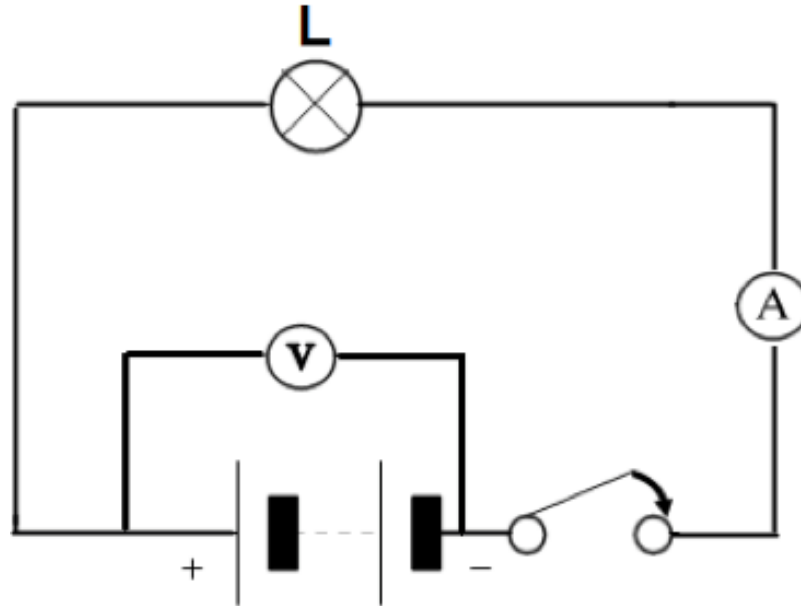- ☐ A Terminal Voltage
- ☐ B EMF
- ☐ C Current
- ☐ D Resistance
- ☐ E Power




**Answer**

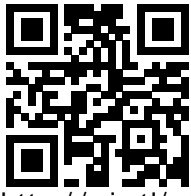


55 A 6V battery, whose internal resistance  $1.5\ \Omega$  is connected in series to a light bulb with a resistance of  $6.8\ \Omega$ . What is the current in the circuit?

**Answer**

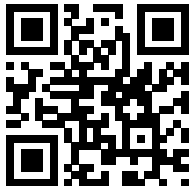

56 A 6V battery, whose internal resistance  $1.5\Omega$  is connected in series to a light bulb with a resistance of  $6.8\Omega$ . What is the terminal voltage of the battery?

**Answer**

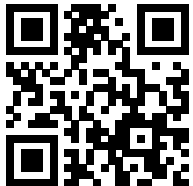

<http://njc.tl/on>

57 A  $25\ \Omega$  resistor is connected across the terminals of a battery whose internal resistance is  $0.6\ \Omega$ . What is the EMF of the battery if the current in the circuit is  $0.75\ \text{A}$ ?

**Answer**

