



Series Circuits

PSI Physics

Name _____

Date: _____ Period: _____

Objectives:


- Measure and calculate voltage drops across any part of a series circuit
- Measure and calculate the current through any part of a series circuit
- Find the equivalent resistance for a series circuit

Materials:




- Battery (or DC Power Source)
- Connecting wires
- Two resistors
- Knife switch
- Ammeter
- Voltmeter

Series Circuits

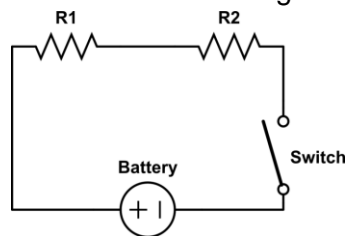Series circuits are circuits where all the resistors are along one path that has no branches.



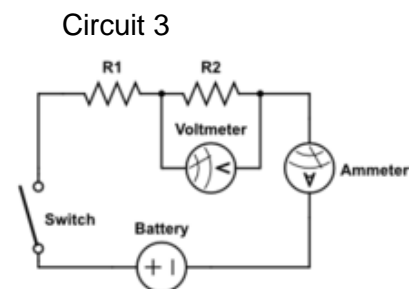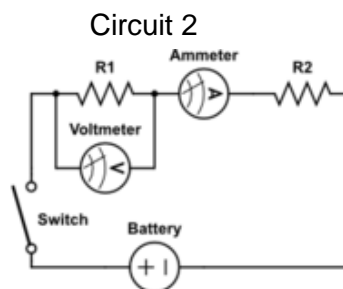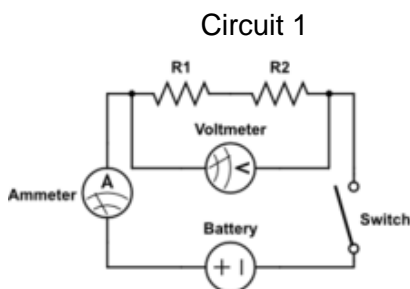Procedure: For each of circuits 1, 2 and 3 below:



1. Construct the circuit. Make sure that the ammeter is in line with the resistors, and that the voltmeter is connected as shown.
2. Record the current and voltage drops.

Data:

Circuit 1		Circuit 2		Circuit 3	
I	V	I_1	V_1	I_2	V_2



Series Circuits

PSI Physics

Analysis:

Use Ohm's Law to calculate the resistance for each circuit.

Resistances		
Circuit 1	Circuit 2	Circuit 3
$R_{\text{equivalent}} = \frac{V}{I}$	$R_1 = \frac{V_1}{I_1}$	$R_2 = \frac{V_2}{I_2}$

Use the information in the Data Collection and Analysis Tables to answer the following questions:

1. How is the current, I , related to the other two currents, I_1 and I_2 ? Write an equation that describes the relationship.
2. How is the voltage, V , related to the other two voltage drops, V_1 and V_2 ? Write an equation that describes the relationship.
3. How is the equivalent resistance, $R_{\text{equivalent}}$, related to the two resistances, R_1 and R_2 ? Write an equation that describes the relationship.
4. A 9V battery is connected to two resistors in series ($R_1 = 12 \Omega$ and $R_2 = 33 \Omega$).
 - a. What is the equivalent resistance, $R_{\text{equivalent}}$, for the circuit?
 - b. What is the current, I , through the circuit? (use $V = IR$)
 - c. What is the voltage drop, V_1 , across resistor R_1 ? (use $V = IR$)



Series Circuits

PSI Physics

5. If you add a third resistor in series with the other two...
- Will $R_{\text{equivalent}}$, increase, decrease or stay the same? Why?
 - Write the equation for $R_{\text{equivalent}}$ for three resistances (R_1 , R_2 , and R_3) in series.
 - Does V , the voltage drop across all the resistors, increase, decrease or stay the same? Why?
 - Does I , the current through the circuit, , increase, decrease or stay the same? Why?
 - Does the voltage drop across R_1 , increase, decrease or stay the same? Why?